

Lab 7: Single-Cycle Processor

Digital Design and Computer Architecture: RISC-V Edition (Harris & Harris, Elsevier © 2021)

Objective

In this lab, you will extend the single-cycle RISC-V processor from the textbook and lecture to support two additional instructions: lui and xor.

1. Single-cycle RISC-V Processor

Figure 1 shows the complete single-cycle processor from the textbook. Figure 2 shows the Control Unit, and Figure 3 shows the ALU. Tables 1 and 2 are the Main Decoder and ALU Decoder truth tables. Table 3 lists the ImmSrc encoding. Figure 4 shows the test program for the RISC-V single-cycle processor in the textbook.

Hint

You can download the sample code and finish this lab by sample code.

What to Turn In

(Make sure your code can read the *riscvtest.s* file. We will grade this lab by our *riscvtest.s* file. Therefore, if your code cannot load *riscvtest.s*, you will have no grade for this lab.)

1. Please indicate how many hours you spent on this lab. This will be helpful for calibrating the workload for next time the course is taught.
2. A marked-up version of Figure 1 (single-cycle processor) showing the needed modifications (lui and xor)
3. A marked-up version of Figures 2 and 3 (if modified) showing the needed modifications for the additional instructions (lui and xor)
4. Amended Main Decoder, ALU Decoder, and ImmSrc truth tables to support lui and xor
5. Amended SystemVerilog code to add support for lui and xor
6. Modified test program that uses lui and xor
7. Simulation waveforms (in the order listed above: clk, reset, PC, Instr, SrcA, SrcB, ALUResult, DataAdr, WriteData, and MemWrite – all displayed in hexadecimal for ease of reading). Does your system pass your testbench? Circle or highlight the waves showing that the correct value is written to the correct address, and make sure it is legible.
8. RTL Viewer schematics.

Please indicate any bugs you found in this lab manual, or any suggestions you would have to improve the lab.

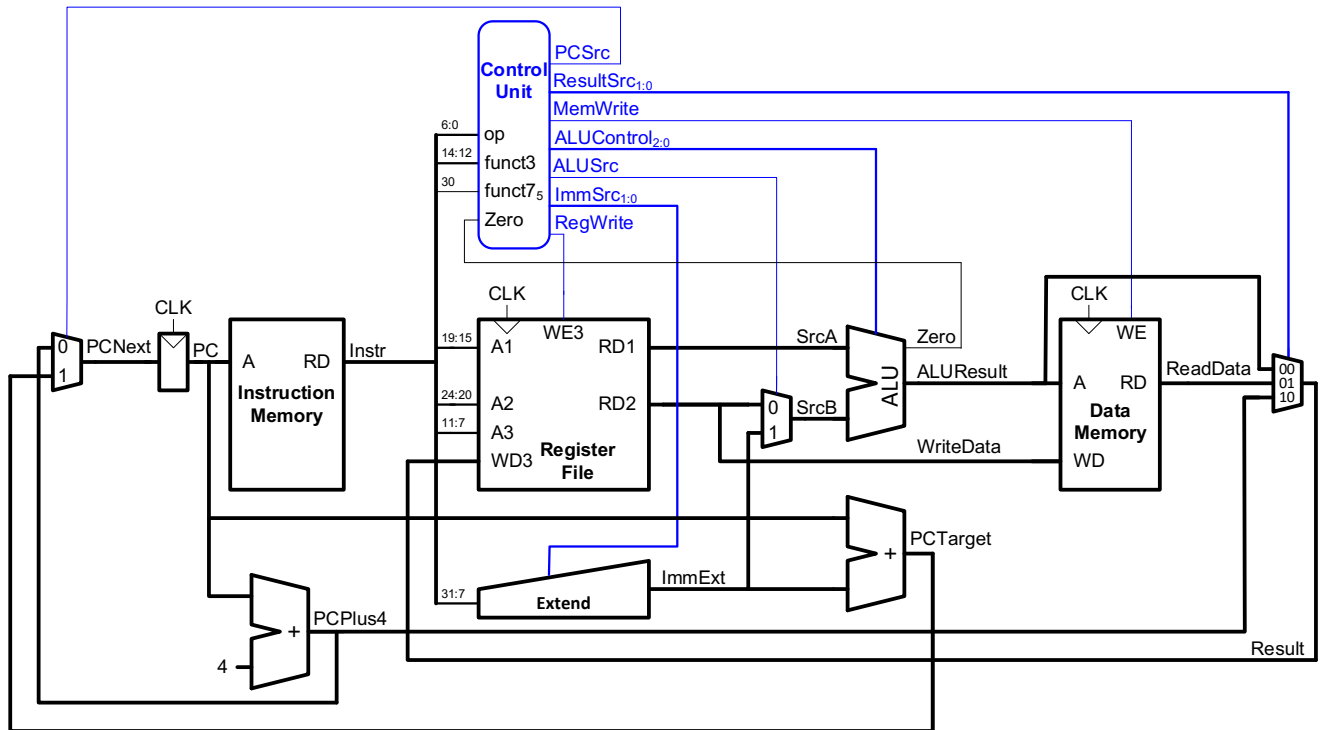


Figure 1: RISC-V single-cycle processor

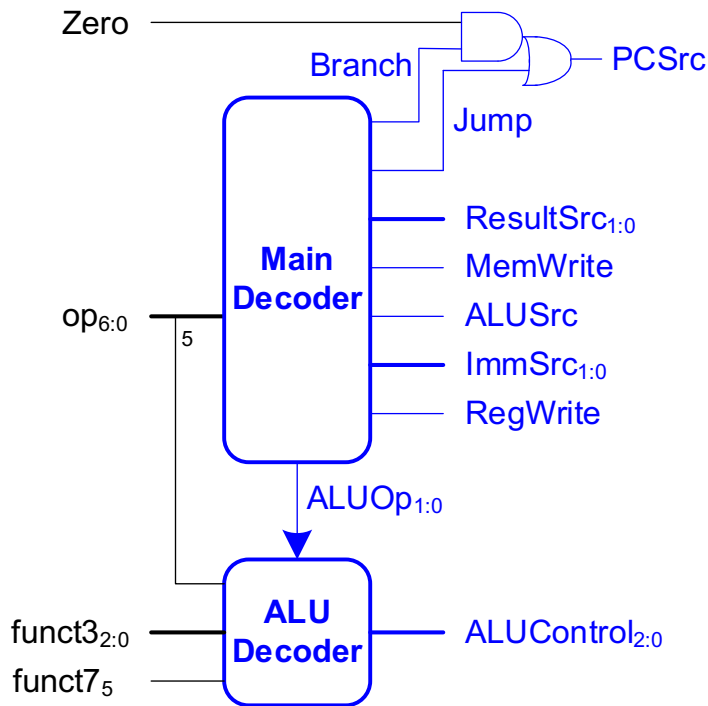


Figure 2: RISC-V single-cycle processor control unit

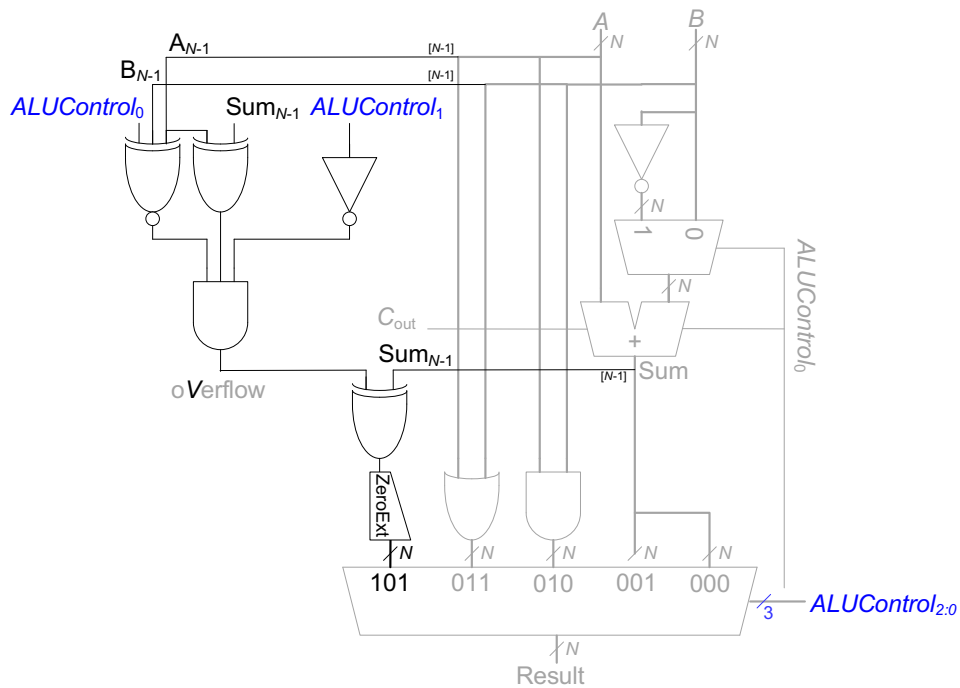


Figure 3: ALU

Table 1. Main Decoder Truth Table

Instruction	Opcode	RegWrite	ImmSrc	ALUSrcA	ALUSrcB	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw	0000011	1	00	0	1	0	01	0	00	0
sw	0100011	0	01	0	1	1	xx	0	00	0
R-type	0110011	1	xx	0	0	0	00	0	10	0
beq	1100011	0	10	0	0	0	xx	1	01	0
I-type ALU	0010011	1	00	0	0	0	00	0	10	0
jal	1101111	1	11	x	x	0	10	0	xx	1

Table 2. ALU Decoder Truth Table

$ALUOp_{1:0}$	$func_{32:0}$	$\{ops, func_{75}\}$	$ALUControl_{2:0}$	Operation
00	x	x	000	Add
01	x	x	001	Subtract
10	000	00, 01, 10	000	Add
	000	11	001	Subtract
	010	x	101	SLT
	110	x	011	OR
	111	x	010	AND

Table 3. ImmSrc encoding

ImmSrc	ImmExt	Type	Description
00	$\{\{20\{Instr[31]\}\}, Instr[31:20]\}$	I	12-bit signed immediate
01	$\{\{20\{Instr[31]\}\}, Instr[31:25], Instr[11:7]\}$	S	12-bit signed immediate
10	$\{\{20\{Instr[31]\}\}, Instr[7], Instr[30:25], Instr[11:8], 1'b0\}$	B	13-bit signed immediate
11	$\{\{12\{Instr[31]\}\}, Instr[19:12], Instr[20], Instr[30:21], 1'b0\}$	J	21-bit signed immediate

	#	RISC-V Assembly	Description	Address	Machine
1	#				
2	main:	addi x2, x0, 5	# x2 = 5	0	00500113
3		addi x3, x0, 12	# x3 = 12	4	00C00193
4		addi x7, x3, -9	# x7 = (12 - 9) = 3	8	FF718393
5		or x4, x7, x2	# x4 = (3 OR 5) = 7	C	0023E233
6		and x5, x3, x4	# x5 = (12 AND 7) = 4	10	0041F2B3
7		add x5, x5, x4	# x5 = (4 + 7) = 11	14	004282B3
8		beq x5, x7, end	# shouldn't be taken	18	02728863
9		slt x4, x3, x4	# x4 = (12 < 7) = 0	1C	0041A233
10		beq x4, x0, around	# should be taken	20	00020463
11		addi x5, x0, 0	# shouldn't happen	24	00000293
12	around:	slt x4, x7, x2	# x4 = (3 < 5) = 1	28	0023A233
13		add x7, x4, x5	# x7 = (1 + 11) = 12	2C	005203B3
14		sub x7, x7, x2	# x7 = (12 - 5) = 7	30	402383B3
15		sw x7, 84(x3)	# [96] = 7	34	0471AA23
16		lw x2, 96(x0)	# x2 = [96] = 7	38	06002103
17		add x9, x2, x5	# x9 = (7 + 11) = 18	3C	005104B3
18		jal x3, end	# jump to end, x3 = 0x44	40	008001EF
19		addi x2, x0, 1	# shouldn't happen	44	00100113
20	end:	add x2, x2, x9	# x2 = (7 + 18) = 25	48	00910133
21		sw x2, 0x20(x3)	# mem[100] = 25	4C	0221A023
22	done:	beq x2, x2, done	# infinite loop	50	00210063

Figure 4. RISC-V test program